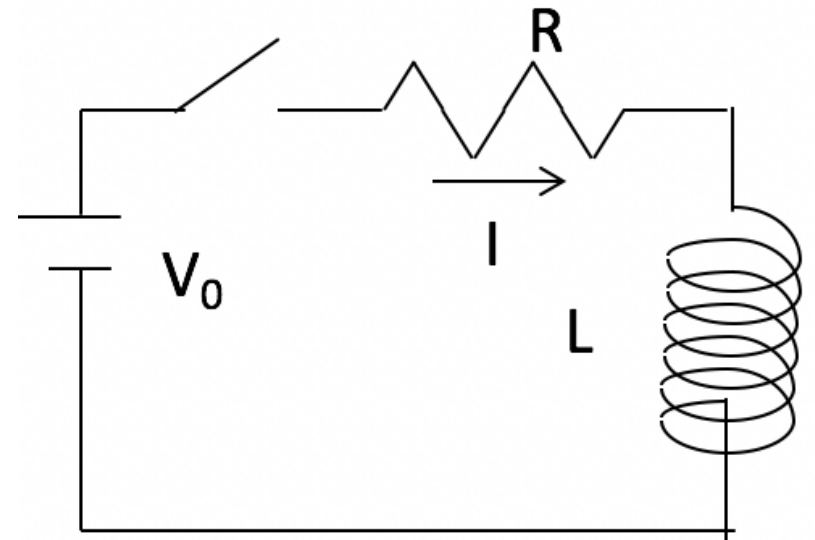







The switch is closed at  $t = 0$ . What can you say about  $I(t = 0+)$ ?

- A. Zero
- B.  $V_0/R$
- C.  $V_0/L$
- D. Something else!
- E. ???




The switch is closed at  $t = 0$ . Which graph best shows  $I(t)$  through the resistor?

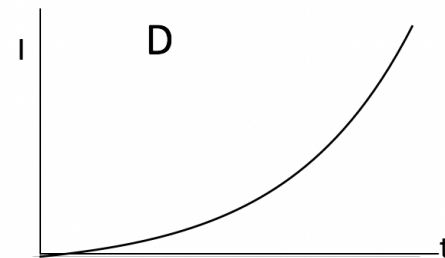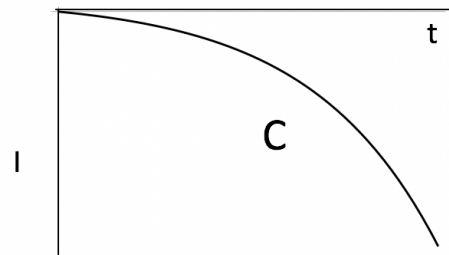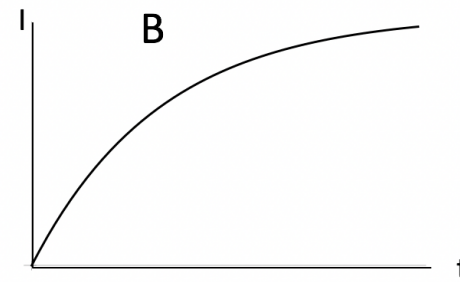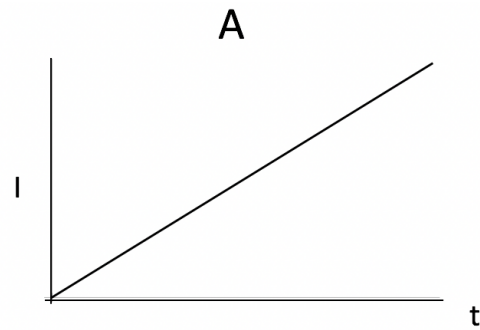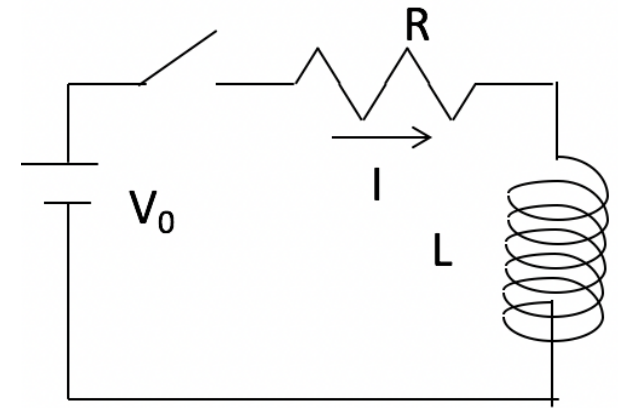E) None of these (they all have a serious error!)



The switch is closed at  $t = 0$ . What can you say about the magnitude of  $\Delta V$  (across the inductor) at  $(t = 0+)$ ?

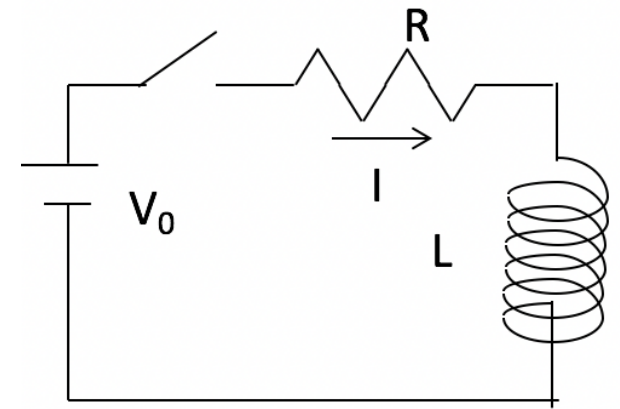- A. Zero
- B.  $V_0$
- C.  $L$
- D. Something else!
- E. ???



The complex exponential:  $e^{i\omega t}$  is useful in calculating properties of many time-dependent equations. According to Euler, we can also write this function as:

A.  $\cos(i\omega t) + \sin(i\omega t)$

B.  $\sin(\omega t) + i \cos(\omega t)$

C.  $\cos(\omega t) + i \sin(\omega t)$

D. MORE than one of these is correct

E. None of these is correct!

What is  $|2 + i|$ ?

A. 1

B.  $\sqrt{3}$

C. 5

D.  $\sqrt{5}$

E. Something else!

What is  $(1 + i)^2/(1 - i)$ ?

A.  $e^{i\pi/4}$

B.  $\sqrt{2}e^{i\pi/4}$

C.  $e^{i3\pi/4}$

D.  $\sqrt{2}e^{i3\pi/4}$

E. Something else!

For the RL circuit with driving voltage of  $V(t) = V_0 \cos(\omega t)$ , we found a solution for the current as a function of time, with  $I = 0$  at  $t = 0$ ,

$$I(t) = a \cos(\omega t + \phi) - a \cos(\phi) e^{-Rt/L}$$

where  $a = \frac{V_0}{\sqrt{R^2 + L^2 \omega^2}}$  and  $\phi = \tan^{-1}(-L\omega/R)$ . What happens to the current when  $\omega \rightarrow \infty$ ?

- A. Current is essentially zero, for all time
- B. Current dies off completely, eventually goes to zero
- C. Eventually, current is constant,  $V_0/R$
- D. It depends
- E. ???